

LM555 TIMER CIRCUIT GROUP PROJECT

- ÖMER EGE NİŞLİ 2024502054
- ÇAĞRI CAN 2024502030


COURSE: EED 1009

JANUARY 10TH, 2025

WHAT WE'LL BE GOING THROUGH IN THIS PRESENTATION:

*Information about LM555 and other components

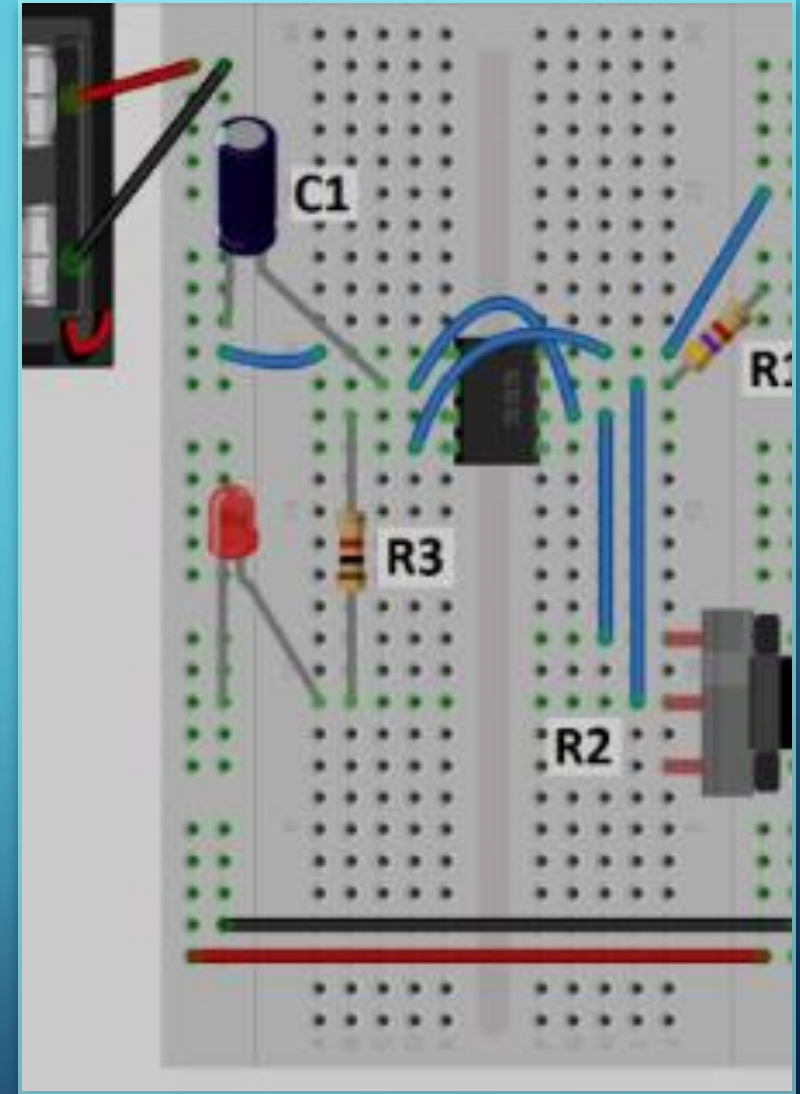- Information about the design of our circuit
- How we chose the circuit elements for this project
- Values of the circuit elements we've used
- Problems we've faced
- Budget analysis of the circuit
- Conclusion
- References




INFORMATION ABOUT LM555

- **LM555** : Widely used in Engineering and very versatile.
- **Modes:** **Astable**, Monostable, Bistable
- **Application:** Used in timing and wave generation




INFORMATION ABOUT OTHER COMPONENTS

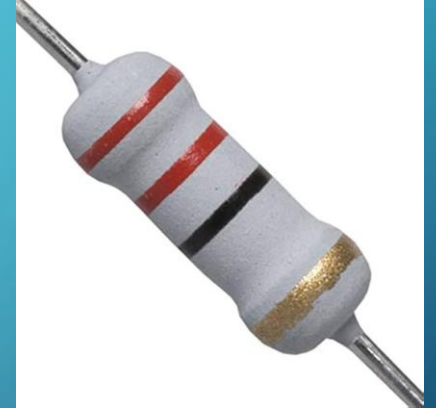- Resistors and capacitors: Key components for tuning circuit parameters.
- Potentiometer: Adjusts frequency in astable mode.
- Battery: Provides voltage to the circuit
- LED : Outputs light



INFORMATION ABOUT THE DESIGN OF THE CIRCUIT

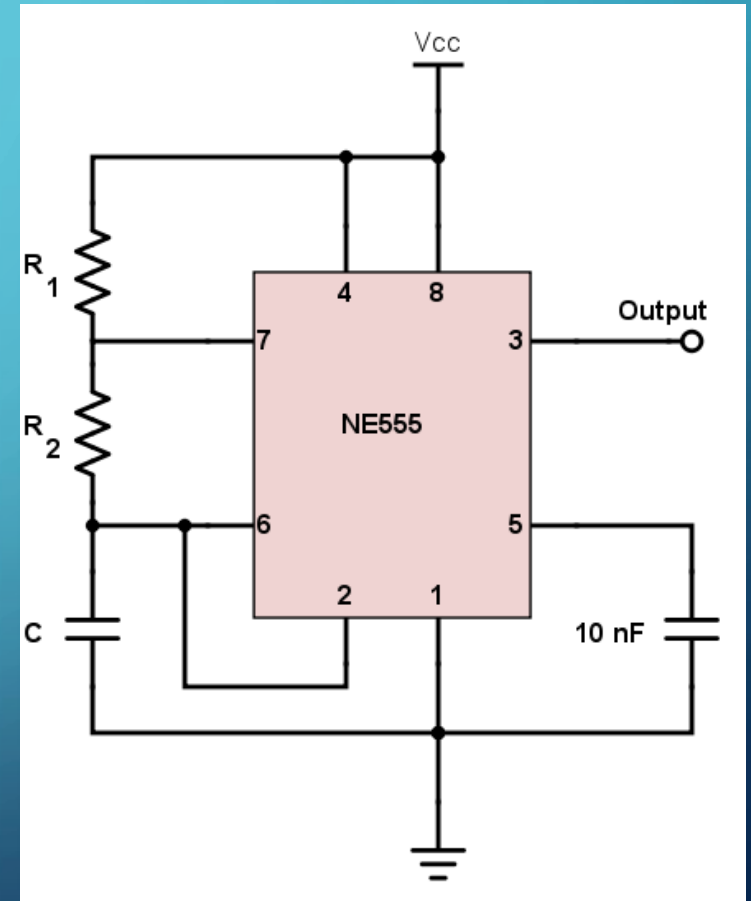- LM555 configured in astable mode for continuous output.
- Generates a square wave to control LED blinking.
- A simple, functional design for visualizing frequency changes.
- The circuit diagram is shown for a better understanding.



CHOOSING CIRCUIT ELEMENTS

- LM555 IC: Easy to use and widely available.
- Resistors and capacitor: Calculated for the desired frequency.
- Potentiometer: Allows real-time frequency adjustment.
- LED: Chosen to visually display the output signal.
- Power source: Selected to match LM555's voltage range




CIRCUIT ELEMENTS VALUES

$$T = \frac{1}{f} = 0.694(R_1 + 2R_2)C$$

- Resistors: 1.6k Ω
- Capacitor: 25 V 47 μ F
- Potentiometer: 10k Ω (adjustable)
- Power supply: 9V DC

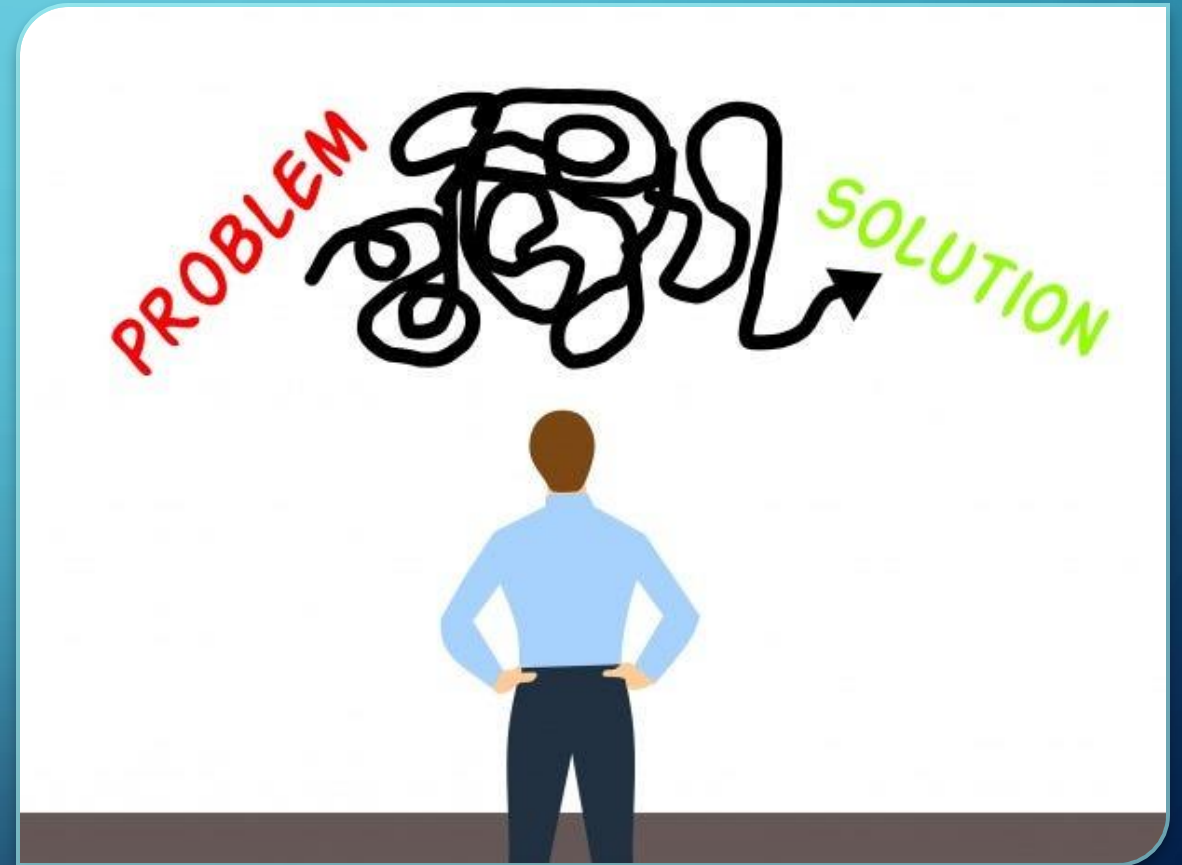PROBLEMS WE'VE FACED

- Being unable to light the LED lamp
Camera not being able to capture the change in period
- LED lamp exploding due to high current



BUDGET

- Total cost: 120฿
- Reusable components: LM555 IC, breadboard, wires.
- Consumables: Resistors, capacitors, and LED.
- Economical design with potential for reuse.



CONCLUSION

- The LM555 IC helped us create a
- Variable - period LED circuit.
- We learned how to design and troubleshoot circuits.
- This project showed how theory can be applied in practice.

**ALL
IN ALL**



THANK YOU FOR LISTENING!



REFERENCES

- 555 Timer Astable Circuit," AllAboutCircuits.com
- 555 Timer Basics," CircuitBasics.com